


Lab 1

 


Inverter Schematic

 


Transient Simulation of schematic

 

 




DRC no errors

 

Lvs Report



QRC report

 

Layout Transient Simulation