
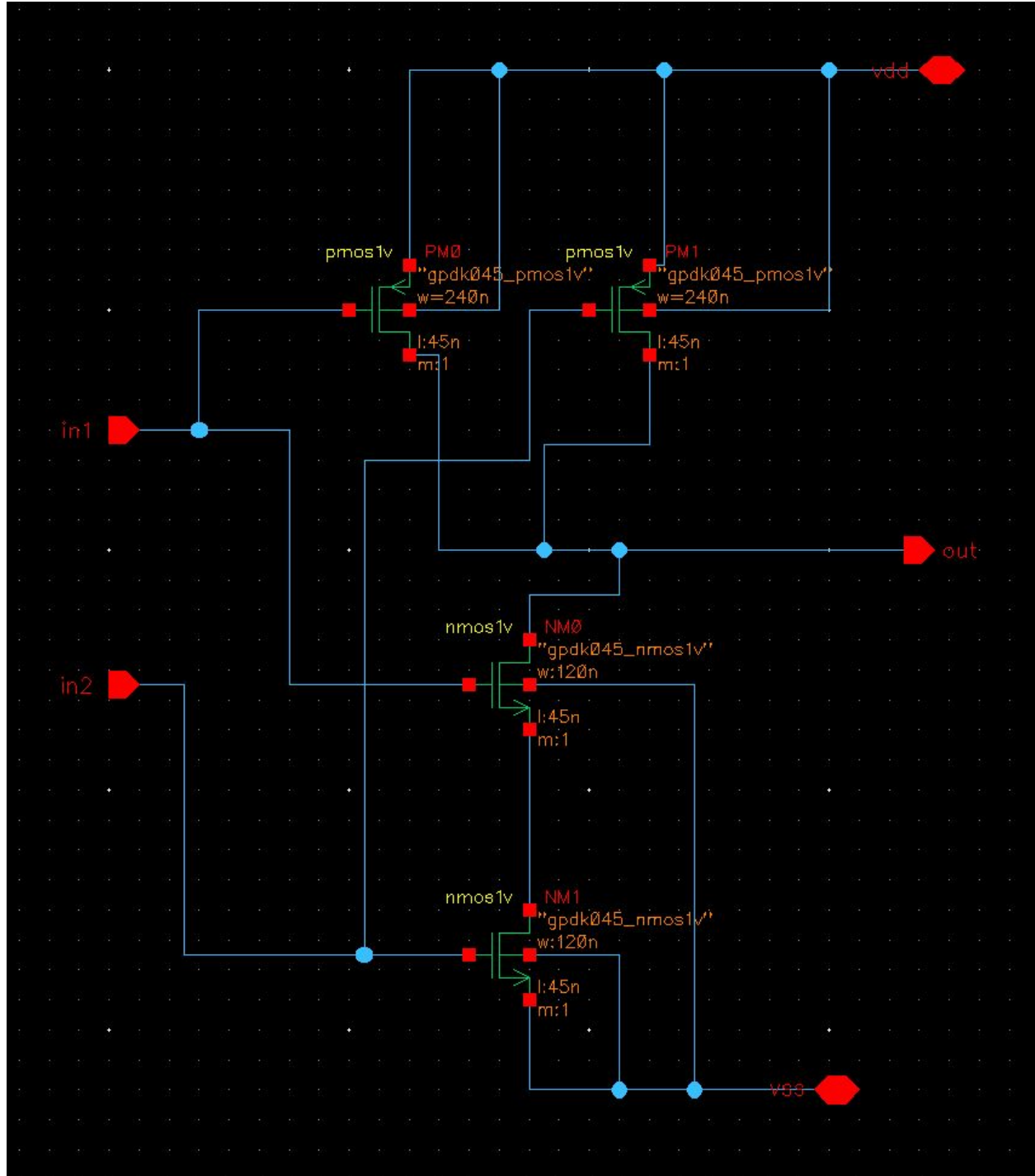


Bradley Newby
ECE 423
November 18th, 2020


Lab 2

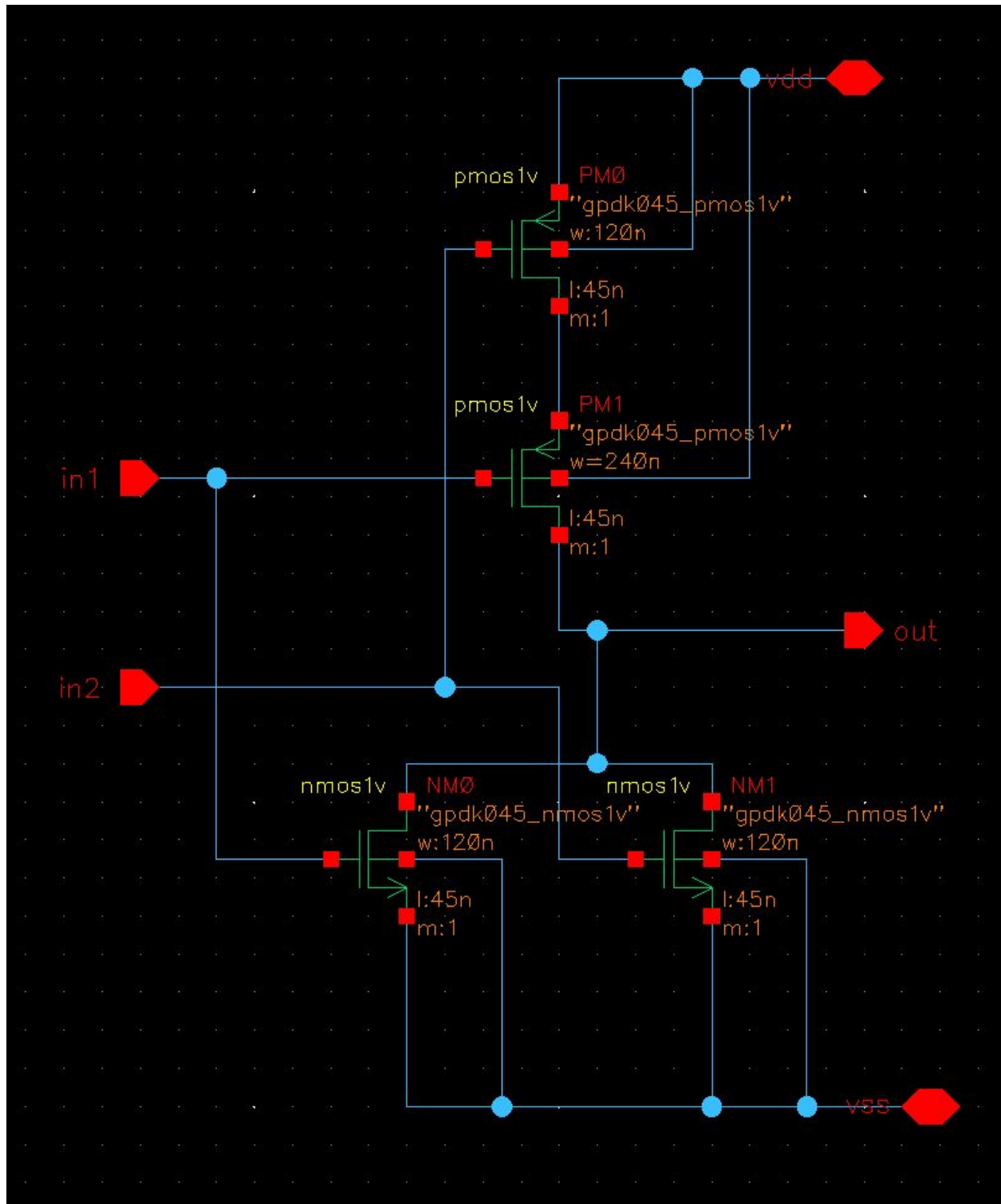


Nand Schematic




NOR Schematic

 


NAND Transient Analysis

 


NOR Transient Analysis

 


Nand Layout

 

NOR Layout

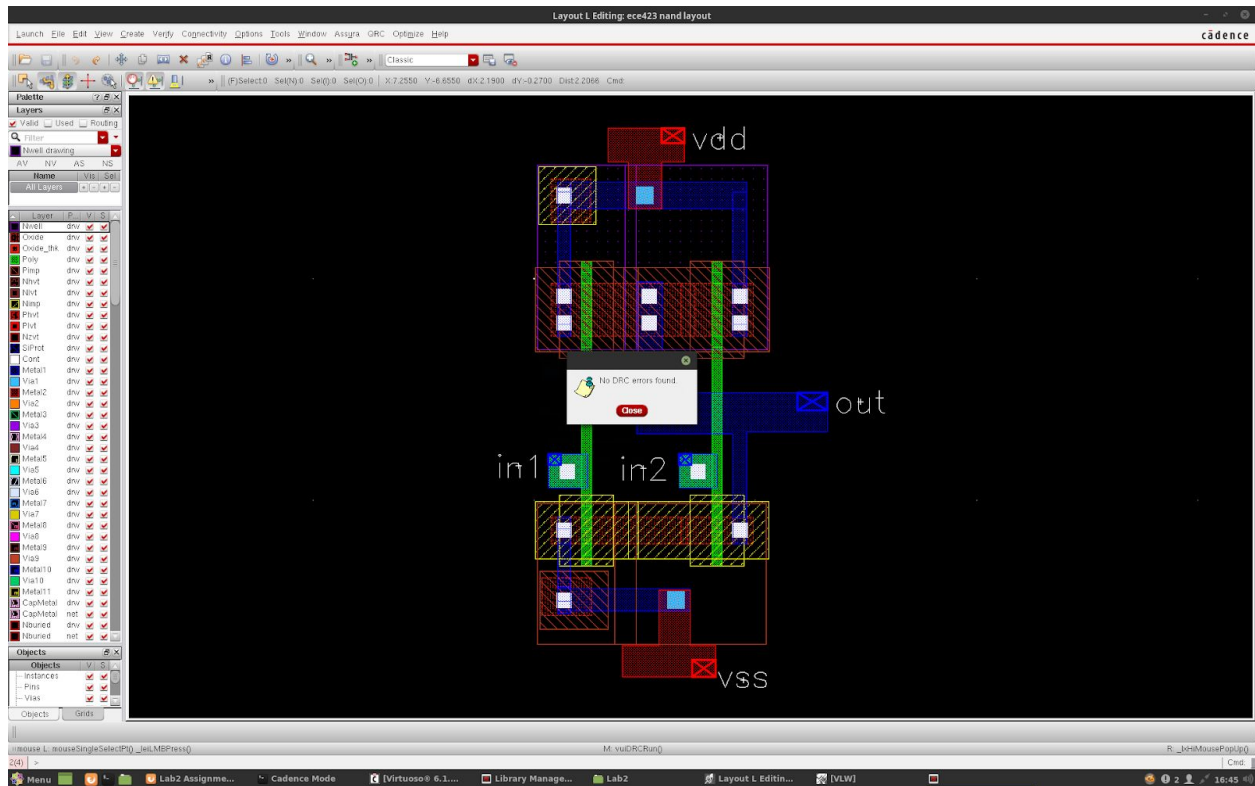

NAND DRC

 

NOR DRC

```

*****
***** nand schematic ece423 <vs> nand layout ece423
*****

```

Filter/Reduce statistics only. Network matching was OK.

Pre-expand Statistics

	Original	
Cell/Device	schematic	layout
(nmos1v) MOS	2	2
(pmos1v) MOS	2	2
	-----	-----
Total	4	4

Reduce Statistics

	Original		Reduced	
Cell/Device	schematic	layout	schematic	layout
(nmos1v) MOS	2	2	0	0
(pmos1v) MOS	2	2	0	0
(nmos1v:SerMos2#1) MosBlk	-	-	1	1
(pmos1v:ParMos2#1) MosBlk	-	-	1	1
	-----	-----	-----	-----
Total	4	4	2	2

Schematic and Layout Match

NAND LVS

```
*****
***** nor schematic ece423 <vs> nor layout ece423
*****
```

Filter/Reduce statistics only. Network matching was OK.

Pre-expand Statistics

```
=====
                                Original
Cell/Device                    schematic layout
(nmoslv) MOS                    2         2
(pmoslv) MOS                    2         2
                                -----
Total                           4         4
```

Reduce Statistics

```
=====
                                Original          Reduced
Cell/Device                    schematic layout schematic layout
(nmoslv) MOS                    2         2             0         0
(pmoslv) MOS                    2         2             0         0
(nmoslv:ParMos2#1) MosBlk      -         -             1         1
(pmoslv:SerMos2#1) MosBlk      -         -             1         1
                                -----
Total                           4         4             2         2
```

Schematic and Layout Match

NOR LVS